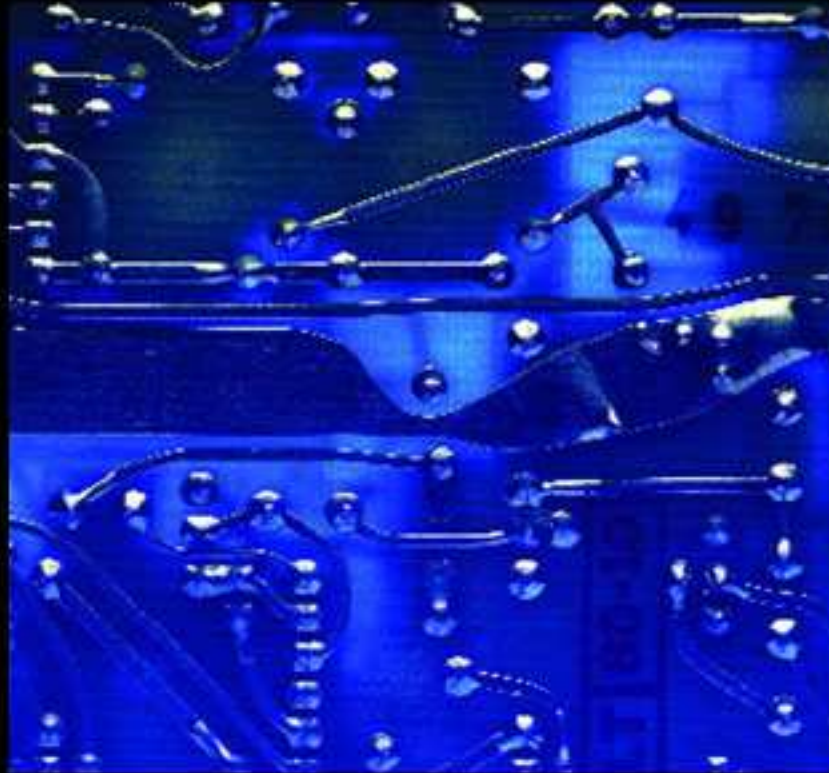


ELECTRONIC DEVICES AND CIRCUIT THEORY

TENTH EDITION

BOYLESTAD



PEARSON

Chapter 3 & 4: Bipolar Junction Transistors and Applications

© Modified by Yuttapong Jiraraksopakun
ENE, KMUTT 2009

Transistor Construction


There are two types of transistors:

- *pnp*
- *npn*


The terminals are labeled:

- **E - Emitter**
- **B - Base**
- **C - Collector**

pnp

 


npn

 

Transistor Operation

With the external sources, V_{EE} and V_{CC} , connected as shown:

 - The emitter-base junction is forward biased
- The base-collector junction is reverse biased




Currents in a Transistor

Emitter current is the sum of the collector and base currents:


$$I_E = I_C + I_B$$

The collector current is comprised of two currents:
 
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$



Common-Base Configuration

 


The base is common to both input (emitter–base) and output (collector–base) of the transistor.

Common-Base Amplifier

Input Characteristics

 
This curve shows the relationship between of input current (I_E) to input voltage (V_{BE}) for three output voltage (V_{CB}) levels.



Common-Base Amplifier

Output Characteristics

 This graph demonstrates the output current (I_C) to an output voltage (V_{CB}) for various levels of input current (I_E).



$$I_{CO} = I_{CBO}$$

Operating Regions

- **Active** – Operating range of the amplifier.
- **Cutoff** – The amplifier is basically off. There is voltage, but little current.
- **Saturation** – The amplifier is full on. There is current, but little voltage.

Regions	Base-Emitter	Collector-Base
Active	Forward-biased	Reverse-biased
Cutoff	Reverse-biased	Reverse-biased
Saturation	Forward-biased	Forward-biased

Approximations

Emitter and collector currents:

$$I_C \cong I_E$$

Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$

Alpha (α)

Alpha (α) is the ratio of I_C to I_E :

$$\alpha_{dc} = \frac{I_C}{I_E}$$

Ideally: $\alpha = 1$

In reality: α is between 0.9 and 0.998

$$I_C = \alpha I_E + I_{CBO}$$


Alpha (α) in the AC mode:

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{constant}}$$

Transistor Amplification

Omit DC biasing to demonstrate AC response

 Assume R_i and R_o from input & output characteristic curves



Currents and Voltages:

$$I_E = I_i = \frac{V_i}{R_i} = \frac{200 \text{ mV}}{20 \Omega} = 10 \text{ mA}$$

$$I_C \cong I_E$$

$$I_L \cong I_i = 10 \text{ mA}$$

$$V_L = I_L R = (10 \text{ mA})(5 \text{ k}\Omega) = 50 \text{ V}$$



Voltage Gain:

$$A_v = \frac{V_L}{V_i} = \frac{50 \text{ V}}{200 \text{ mV}} = 250$$

Common–Emitter Configuration


The emitter is common to both input (base-emitter) and output (collector-emitter).

  The input is on the base and the output is on the collector.




(a)

Common-Emitter Characteristics

 

Collector Characteristics

 

Base Characteristics

Common-Emitter Amplifier Currents

Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

Actual Currents

$$I_C = \alpha I_E + I_{CBO} \quad \text{where } I_{CBO} = \text{minority collector current}$$

I_{CBO} is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When $I_B = 0 \mu\text{A}$ the transistor is in cutoff, but there is some minority current flowing called I_{CEO} .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

Beta (β)

β represents the amplification factor of a transistor. (β is sometimes referred to as h_{fe} , a term used in transistor modeling calculations)

In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

In AC mode:


$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

Beta (β)

Determining β from a Graph

$$\begin{aligned}\beta_{AC} &= \frac{(3.2 \text{ mA} - 2.2 \text{ mA})}{(30 \mu\text{A} - 20 \mu\text{A})} \\ &= \frac{1 \text{ mA}}{10 \mu\text{A}} \bigg|_{V_{CE} = 7.5} \\ &= 100\end{aligned}$$

$$\begin{aligned}\beta_{DC} &= \frac{2.7 \text{ mA}}{25 \mu\text{A}} \bigg|_{V_{CE} = 7.5} \\ &= 108\end{aligned}$$

 

Both β values are usually reasonably close and are often used interchangeably

Beta (β)

Relationship between amplification factors β and α


$$\alpha = \frac{\beta}{\beta + 1} \qquad \beta = \frac{\alpha}{\alpha - 1}$$

Relationship Between Currents

$$I_C = \beta I_B \qquad I_E = (\beta + 1)I_B$$


Common-Collector Configuration

 The input is on the base and the output is on the emitter.



Common–Collector Configuration

 The characteristics are similar to those of the common-emitter configuration, except the vertical axis is I_E .




Operating Limits for Each Configuration

V_{CE} is at maximum and I_C is at minimum ($I_{Cmax} = I_{CEO}$) in the cutoff region.

I_C is at maximum and V_{CE} is at minimum ($V_{CEmax} = V_{CEsat} = V_{CEO}$) in the saturation region.

 The transistor operates in the active region between saturation and cutoff.



Power Dissipation

Common-base:

$$P_{Cmax} = V_{CB}I_C$$

Common-emitter:

$$P_{Cmax} = V_{CE}I_C$$

Common-collector:

$$P_{Cmax} = V_{CE}I_E$$


Transistor Specification Sheet

MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	V_{CE0}	30	Vdc
Collector-Base Voltage	V_{CB0}	40	Vdc
Emitter-Base Voltage	V_{EB0}	5.0	Vdc
Collector Current – Continuous	I_C	200	mA dc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/°C
Operating and Storage Junction Temperature Range	T_J, T_{stg}	-55 to +150	°C

THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	°C/W
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	°C/W

 


Transistor Specification Sheet

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Collector-Emitter Breakdown Voltage (1) ($I_C = 1.0\text{ mAdc}$, $I_E = 0$)	$V_{(BR)CEO}$	30		Vdc
Collector-Base Breakdown Voltage ($I_C = 10\text{ }\mu\text{Adc}$, $I_E = 0$)	$V_{(BR)CBO}$	40		Vdc
Emitter-Base Breakdown Voltage ($I_E = 10\text{ }\mu\text{Adc}$, $I_C = 0$)	$V_{(BR)EBO}$	5.0	–	Vdc
Collector Cutoff Current ($V_{CE} = 20\text{ Vdc}$, $I_E = 0$)	I_{CBO}	–	50	nAdc
Emitter Cutoff Current ($V_{BE} = 3.0\text{ Vdc}$, $I_C = 0$)	I_{EBO}	–	50	nAdc
ON CHARACTERISTICS				
DC Current Gain(1) ($I_C = 2.0\text{ mAdc}$, $V_{CE} = 1.0\text{ Vdc}$) ($I_C = 50\text{ mAdc}$, $V_{CE} = 1.0\text{ Vdc}$)	h_{FE}	50 25	150 –	–
Collector-Emitter Saturation Voltage(1) ($I_C = 50\text{ mAdc}$, $I_B = 5.0\text{ mAdc}$)	$V_{CE(sat)}$	–	0.3	Vdc
Base-Emitter Saturation Voltage(1) ($I_C = 50\text{ mAdc}$, $I_B = 5.0\text{ mAdc}$)	$V_{BE(sat)}$	–	0.95	Vdc
SMALL-SIGNAL CHARACTERISTICS				
Current-Gain – Bandwidth Product ($I_C = 10\text{ mAdc}$, $V_{CE} = 20\text{ Vdc}$, $f = 100\text{ MHz}$)	f_T	250		MHz
Output Capacitance ($V_{CE} = 5.0\text{ Vdc}$, $I_E = 0$, $f = 100\text{ MHz}$)	C_{rbo}	–	4.0	pF
Input Capacitance ($V_{BE} = 0.5\text{ Vdc}$, $I_C = 0$, $f = 100\text{ kHz}$)	C_{ibo}	–	8.0	pF
Collector-Base Capacitance ($I_E = 0$, $V_{CB} = 5.0\text{ V}$, $f = 100\text{ kHz}$)	C_{cb}	–	4.0	pF
Small-Signal Current Gain ($I_C = 2.0\text{ mAdc}$, $V_{CE} = 10\text{ Vdc}$, $f = 1.0\text{ kHz}$)	h_{fe}	50	200	–
Current Gain – High Frequency ($I_C = 10\text{ mAdc}$, $V_{CE} = 20\text{ Vdc}$, $f = 100\text{ MHz}$) ($I_C = 2.0\text{ mAdc}$, $V_{CE} = 10\text{ V}$, $f = 1.0\text{ kHz}$)	h_{fe}	2.5 50	– 200	–
Noise Figure ($I_C = 100\text{ }\mu\text{Adc}$, $V_{CE} = 5.0\text{ Vdc}$, $R_S = 1.0\text{ k ohm}$, $f = 1.0\text{ kHz}$)	NF	–	6.0	dB


(1) Pulse Test: Pulse Width = 300 μs , Duty Cycle = 2.0%

Transistor Terminal Identification

 

Biasing

 Biasing: The DC voltages applied to a transistor in order to turn it on so that it can amplify the AC signal.




$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

Operating Point

 The DC input establishes an operating or *quiescent point* called the *Q-point*.



The Three States of Operation

- **Active or Linear Region Operation**

Base–Emitter junction is forward biased

Base–Collector junction is reverse biased

- **Cutoff Region Operation**

Base–Emitter junction is reverse biased

- **Saturation Region Operation**


Base–Emitter junction is forward biased

Base–Collector junction is forward biased

DC Biasing Circuits

- **Fixed-bias circuit**
- **Emitter-stabilized bias circuit**
- **Collector-emitter loop**
- **Voltage divider bias circuit**
- **DC bias with voltage feedback**

Fixed Bias

 


The Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

 


Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

 

Saturation

When the transistor is operating in saturation, current through the transistor is at its *maximum* possible value.

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C}$$

$$V_{CE} \cong 0 \text{ V}$$

This approximation is equivalent to move the region below $V_{CE\text{sat}}$ of the output curves to align on the output current axis.

Load Line Analysis

The end points of the load line are:

$I_{C\text{sat}}$


$$I_C = V_{CC} / R_C$$

$$V_{CE} = 0 \text{ V}$$

$V_{CE\text{cutoff}}$

$$V_{CE} = V_{CC}$$


$$I_C = 0 \text{ mA}$$

 

The Q -point is the operating point:


- where the value of R_B sets the value of I_B
- that sets the values of V_{CE} and I_C

Circuit Values Affect the Q-Point

 


more ...

Circuit Values Affect the Q-Point

 


more ...

Circuit Values Affect the Q-Point

 

Emitter-Stabilized Bias Circuit

 Adding a resistor (R_E) to the emitter circuit stabilizes the bias circuit.



Base-Emitter Loop

From Kirchhoff's voltage law:


$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

Since $I_E = (\beta + 1)I_B$:

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

Solving for I_B :
 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$



Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since $I_E \cong I_C$:


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Also:

$$V_E = I_E R_E$$

$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
 
$$V_B = V_{CC} - I_R R_B = V_{BE} + V_E$$



Improved Biased Stability

Stability refers to a circuit condition in which the currents and voltages will remain fairly constant over a wide range of temperatures and transistor Beta (β) values.

Adding RE to the emitter improves the stability of a transistor.

Fixed-bias circuit

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$



Emitter-stabilized bias circuit

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

$$I_C = \beta I_B$$

I_B in fixed-bias circuit cannot change, so change in β results in large change in output current and voltage.

Saturation Level

  

The endpoints can be determined from the load line.

$V_{CE\text{ cutoff}}:$

$$V_{CE} = V_{CC}$$

$$I_C = 0\text{ mA}$$

$I_{C\text{ sat}}:$


$$V_{CE} = 0\text{ V}$$

$$I_C = \frac{V_{CC}}{R_C + R_E}$$

Voltage Divider Bias

This is a very stable bias circuit.

 The currents and voltages are nearly independent of any variations in β .



Approximate Analysis

Where $I_B \ll I_1$ and $I_1 \cong I_2$:

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Where $\beta R_E > 10R_2$:

$$I_E = \frac{V_E}{R_E}$$


$$V_E = V_B - V_{BE}$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

 

Voltage Divider Bias Analysis

Transistor Saturation Level

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff:

$$V_{CE} = V_{CC}$$
$$I_C = 0\text{mA}$$


Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$
$$V_{CE} = 0\text{V}$$

Voltage Divider Bias

$$V_B = \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$
 
$$= \left(\frac{12 \text{ k}\Omega}{27 \text{ k}\Omega + 12 \text{ k}\Omega} \right) (+15 \text{ V}) = 4.62 \text{ V}$$




V_E is one diode drop less than V_B :

$$V_E = 4.62 \text{ V} - 0.7 \text{ V} = 3.92 \text{ V}$$

Applying Ohm's law:
 
$$I_E = \frac{V_E}{R_E} = \frac{3.92 \text{ V}}{680 \Omega} = 5.76 \text{ mA}$$



Voltage Divider Bias (Exact)


$$V_{TH} = V_{B(\text{no load})}$$

$$= 4.62 \text{ V}$$

$$R_{TH} = R_1 \parallel R_2 =$$

$$= 8.31 \text{ k}\Omega$$

The Thevenin input circuit can be drawn

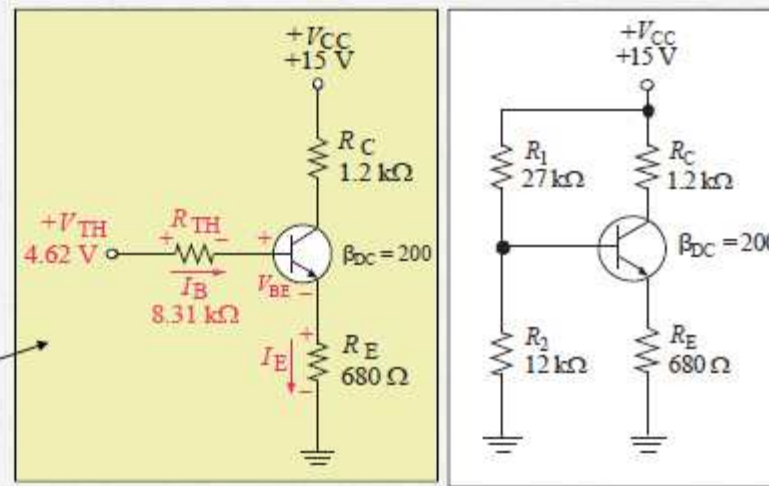


$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$

$$I_E = \frac{V_{TH} - V_{BE}}{R_E + \frac{R_{TH}}{\beta_{DC}}}$$

Substituting and solving,

$$I_E = \frac{4.62 \text{ V} - 0.7 \text{ V}}{680 \Omega + \frac{8.31 \text{ k}\Omega}{200}} = 5.43 \text{ mA}$$

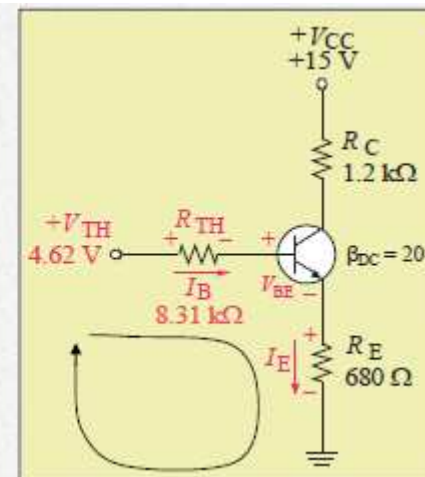
$$\text{and } V_E = I_E R_E = (5.43 \text{ mA})(0.68 \text{ k}\Omega) = 3.69 \text{ V}$$



DC Bias with Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

 In this bias circuit the Q-point is only slightly dependent on the transistor beta, β .



Base-Emitter Loop

From Kirchhoff's voltage law:

$$V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

Where $I_B \ll I_C$:


$$I'_C = I_C + I_B \cong I_C$$

Knowing $I_C = \beta I_B$ and $I_E \cong I_C$, the loop equation becomes:

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

Solving for I_B :
 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$



Collector-Emitter Loop

Applying Kirchoff's voltage law:


$$I_E + V_{CE} + I'_C R_C - V_{CC} = 0$$

Since $I'_C \cong I_C$ and $I_C = \beta I_B$:

$$I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$$

Solving for V_{CE} :

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

 

Base-Emitter Bias Analysis

Transistor Saturation Level

$$I_{C\text{sat}} = I_{C\text{max}} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff:


$$V_{CE} = V_{CC}$$
$$I_C = 0 \text{ mA}$$

Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$
$$V_{CE} = 0 \text{ V}$$

Transistor Switching Networks

 Transistors with only the DC source applied can be used as electronic switches.



Switching Circuit Calculations

Saturation current:

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C}$$


To ensure saturation:

$$I_B > \frac{I_{C\text{sat}}}{\beta_{dc}}$$

Emitter-collector resistance
at saturation and cutoff:

$$R_{\text{sat}} = \frac{V_{CE\text{sat}}}{I_{C\text{sat}}}$$
 
$$R_{\text{cutoff}} = \frac{V_{CC}}{I_{CEO}}$$




Switching Time

Transistor switching times:

$$t_{\text{on}} = t_r + t_d$$

$$t_{\text{off}} = t_s + t_f$$

 

Troubleshooting Hints

- **Approximate voltages**
 - $V_{BE} \cong .7 \text{ V}$ for silicon transistors
 - $V_{CE} \cong 25\% \text{ to } 75\% \text{ of } V_{CC}$
- **Test for opens and shorts with an ohmmeter.**
- **Test the solder joints.**
- **Test the transistor with a transistor tester or a curve tracer.**
- **Note that the load or the next stage affects the transistor operation.**

PNP Transistors

The analysis for *pnp* transistor biasing circuits is the same as that for *npn* transistor circuits. The only difference is that the currents are flowing in the opposite direction.

Homework 3 (Chapter 3)

- **Common-Base Configuration**
 - **3.4 (13)**
- **Transistor Amplifying Action**
 - **3.5 (18)**
- **Common-Emitter Configuration**
 - **3.6 (23)**

Homework 3 (Chapter 4)

- **Fixed-Bias Configuration**
 - **4.3 (1)**
- **Emitter-Bias Configuration**
 - **4.4 (8)**
- **Voltage Divider Configuration**
 - **4.5 (13)**
- **Collector-Feedback Configuration**
 - **4.6 (23)**
- **Miscellaneous Bias Configuration**
 - **4.59 (30)**